

Analysis

Note:

We will reference the nodes in this analysis based on the pins indices of the OP-AMP found in the schematic page.

DC Analysis:

At node 3:

$$\begin{aligned}\frac{v_3 - 0}{R_1} + \frac{v_3 - v_{\text{indc}}}{R_2} &= 0 \\ \Rightarrow v_3 &= \frac{R_1 v_{\text{indc}}}{R_1 + R_2} \\ \text{since : } R_1 &= 3R_2 \\ \Rightarrow v_3 &= \frac{3}{4} v_{\text{indc}}\end{aligned}\tag{1}$$

At node 2:

$$\begin{aligned}\frac{v_2 - 0}{R_4} + \frac{v_2 - v_6}{R_5} &= 0 \\ \Rightarrow v_6 &= \left(\frac{R_5}{R_4} + 1 \right) v_2 \\ \text{But : } R_5 &= R_4 \\ \text{Therefore : } v_6 &= 2v_2\end{aligned}\tag{2}$$

At the output node:

$$\begin{aligned}\frac{v_{\text{outdc}} - v_6}{R_6} + \frac{v_{\text{out}} - 0}{R_L} &= 0 \\ \Rightarrow v_{\text{outdc}} &= \frac{R_L}{R_L + R_6} v_6\end{aligned}\tag{3}$$

Using 1 and 2 we get:

$$v_{\text{outdc}} = \frac{3}{2} \frac{R_L}{R_L + R_6} v_{\text{indc}}\tag{4}$$

Note that : $v_2 = v_3$

AC analysis:

At node 3:

$$\begin{aligned}\frac{v_3 - v_{\text{inac}}}{R_1} + \frac{v_3 - 0}{R_2} &= 0 \\ \Rightarrow v_3 &= \frac{R_2}{R_1 + R_2} v_{\text{inac}} \\ \Rightarrow v_3 &= \frac{1}{4} v_{\text{inac}}\end{aligned}\tag{5}$$

At node 2 we get the same equations as the DC analysis.

Using 2 and the same form of equation 3, we get:

$$v_{\text{outac}} = \frac{1}{2} \frac{R_L}{R_L + R_6} v_{\text{inac}}\tag{6}$$

Combining 6 and 3 we get te overall output voltage:

$$\begin{aligned}v_{\text{out}} &= \frac{1}{2} \frac{R_L}{R_L + R_6} v_{\text{inac}} + \frac{3}{2} \frac{R_L}{R_L + R_6} v_{\text{indc}} \\ \text{Or : } v_{\text{out}} &= \left(\frac{1}{2} v_{\text{inac}} + \frac{3}{2} v_{\text{indc}} \right) \frac{R_L}{R_L + R_6}\end{aligned}$$